

H 1232

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2006.

Fourth Semester

Electronics and Communication Engineering

EC 242 — DIGITAL ELECTRONICS

Time : Three hours

Maximum : 100 marks

Answer ALL questions.

PART A — (10 × 2 = 20 marks)

1. Find the 2's complement and 1's complement of 101101.
2. Simplify $x_1 + x_1x_2$.
3. Write down the characteristics of NMOS logic gates.
4. Write about the WIRED-AND logic in open collector TTL NAND gate.
5. Find the standard sum for the following function
$$f = x_1x_2x_3 + x_1x_3x_4 + x_1x_2x_4.$$
6. Draw a parity checker circuit for 3 bit binary word $x_1x_2x_3$.
7. What is a flip-flop?
8. Differentiate between edge-triggered flip-flop and level triggered flip-flop.
9. What is Race problem in flip-flops?
10. What are the classes of asynchronous sequential circuits?

PART B — (5 × 16 = 80 marks)

11. Design a negative edge triggered T flip flop. The circuit has two inputs, T (toggle) and C (clock) and outputs Q and \bar{Q} . The output state is complemented if $T = 1$ and the clock C changes from 1 to 0. Otherwise under any other input condition, the output Q remains unchanged.

12. (a) (i) Prove the Demorgan's laws using Boolean algebra. (8)

(ii) Find the minimal sum of product form for the following switching function

$$f(x_1, x_2, x_3, x_4, x_5) = \sum m(2, 3, 6, 7, 11, 12, 13, 14, 15, 23, 28, 29, 30, 31) \quad (8)$$

Or

(b) Simplify the following Boolean expressions

(i) $(x_1 + x_2)(x_1'x_3' + x_3)(x_2' + x_1x_3)'$. (6)

(ii) Find the minimal-sum-of product expression for the following switching function

$$f(x_1, x_2, x_3, x_4, x_5) = \sum m(1, 2, 3, 6, 8, 9, 14, 17, 24, 25, 26, 27, 30, 31) + \sum d(4, 5). \quad (10)$$

13. (a) (i) Explain the working of a totempole two input TTL NAND gate and analyse its merits and drawbacks if any. (10)

(ii) Define the terms : fan-out, noise margin, propagation delay. (6)

Or

(b) (i) Explain the working of a two input CMOS NAND gate. (6)

(ii) Write notes on ECL, RTL and HTL logic families. (10)

14. (a) (i) Design and explain the working of a mod-9 counter. (10)

(ii) Write notes on memory decoding techniques. (6)

Or

(b) (i) Explain the working of master-slave JK flip flop. State its merit. (8)

(ii) Explain the Read and Write cycles of RAM. (8)

15. (a) Design a BCD to Excess-3 code converter with (i) PLA (ii) PAL devices.

Or

(b) Design and explain

(i) 4 bit magnitude comparator

(ii) priority encoder.