

K 243

B.E/B.TECH DEGREE EXAMINATIONS NOV/DEC 2010

THIRD SEMESTER

ELECTRONICS AND COMMUNICATION ENGINEERING

EC1203—DIGITAL ELECTRONICS

(Common to Mechanical Engineering)

(REGULATIONS 2007)

Time : Three hours

Maximum : 100 marks

Answer all the questions

Part – A (10 x 2 = 20)

1. What is the major difference between ECL and TTL?
2. What is enhancement mode operation of MOS?
3. How will you build a full adder using two half adders and an OR gate?
4. Draw the block diagram of a two bit parallel adder.
5. Obtain 8x1 MUX using dual 4x1 MUX.
6. How many address lines are required for a 4K ROM?
7. Distinguish Mealy and Moore machines.
8. What is the basic difference between a Johnson counter and a ring counter?
9. Compare fundamental and pulse mode asynchronous sequential circuit.
10. Define races in asynchronous sequential circuit.

K 243

Part - B (5 x 16 = 80)

11. a. Draw and explain the circuit diagram of a TTL NAND gate with totem-pole and open collector output. (16)
- Or
- b. (i) With neat diagram explain RTL NOR gate. Also discuss about the characteristics of RTL family. (8)
- (ii) Draw the basic CMOS inverter and explain its operation. (8)
12. a. i. Design a magnitude comparator such that it compares two 2-bit numbers A and B. (8)
- ii. Design a full adder circuit using basic gates. (8)
- Or
- b. Design a BCD adder using full-adders and explain its operation. (16)
13. a. Design a logic circuit to convert the Gray code to binary code. (16)
- Or
- b. i. Using 8x1 multiplexer realize the following Boolean function (8)
- $$F(w,x,y,z) = \Sigma(0,1,2,4,5,7,8,9,12,13)$$

- ii. Implement the following two Boolean (8)
functions with a PLA

$$F(A,B,C) = \Sigma(0,1,2,4)$$

$$F(A,B,C) = \Sigma(0,5,6,7)$$

14. a. Design a 4-bit self correcting ring counter (16)
using D flip-flop.

Or

- b. Design a synchronous MOD-16 counter (16)
using J-K flip-flops.

15. a. i. What is meant by hazard? Discuss the (6)
types of hazards.

- ii. With suitable example explain how static, (10)
dynamic and essential hazards can be
eliminated.

Or

- b. Design an asynchronous sequential (16)
circuit with two inputs X_1 and X_2 and one
output Z . Initially both inputs are equal to
zero. When X_1 or X_2 becomes '1' and
output Z becomes 1. When the second
input also becomes 1, the output changes
to 0. The output stays at 0 until the circuit
goes back to the initial state.